



Next: [About this document ...](#) Up: [midterm2_18f](#) Previous: [Instructions](#)

Do not click until you are ready to take the exam


The Problems

1. Problem 12 (33 points)

The circuit given below is composed of a differential amplifier (top) and a voltage follower (bottom), which feeds the output v_{out} to the non-inverting input of the differentiator.

Give the expression of the output current \underline{i} , and show that it is uniquely determined by the circuit parameters, independent of the load resistor R_L , i.e., the circuit is a current source.

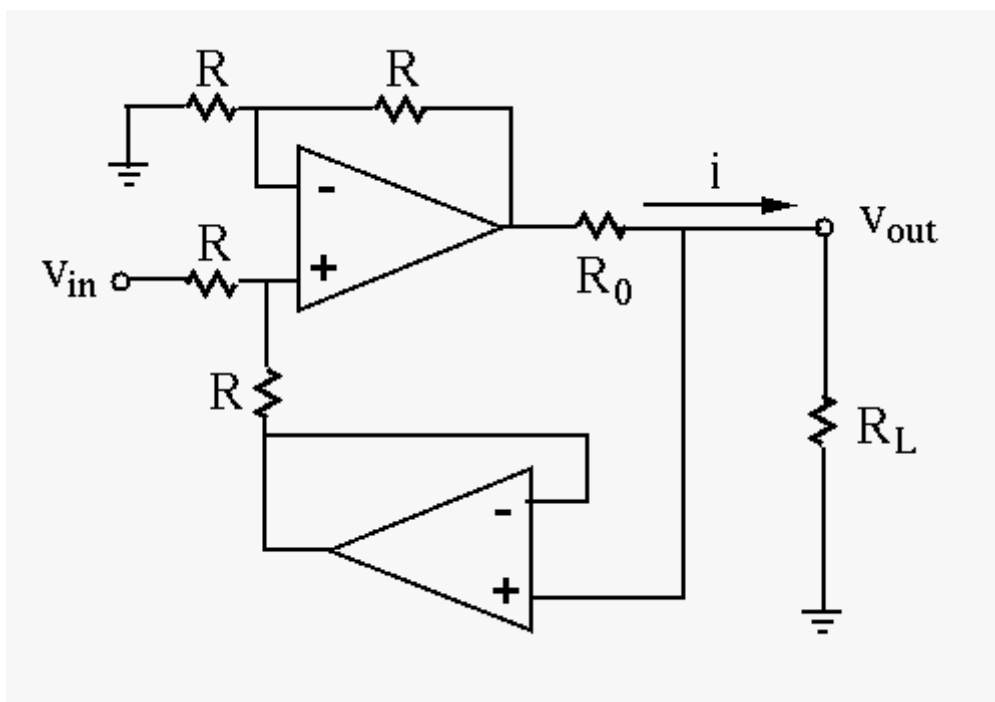
Hint: use virtual ground assumption, label the voltages at both the inverting and non-inverting inputs of the differentiator by V_1 , and label the output of the differentiator as V_2 . Apply KCL to the two input nodes.



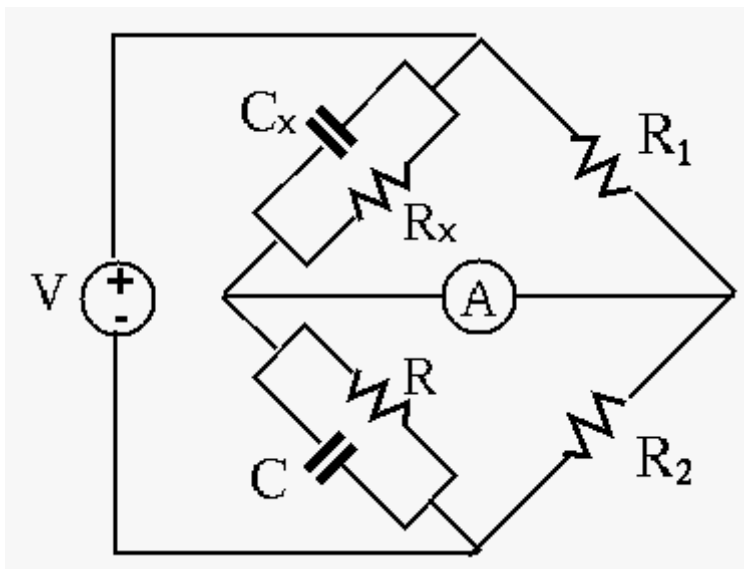2. Problem 2 (33 points)

The AC bridge circuit shown below powered by an AC voltage source is used to measure the unknown capacitance C_x and unknown resistance R_x . By adjusting R_1 or R_2 , the bridge is balanced, i.e., the


current through the ammeter is zero, and the values of C_x and R_x can be expressed in terms of the known values of R , C , R_1 and R_2 . Give these expressions for C_x and R_x .



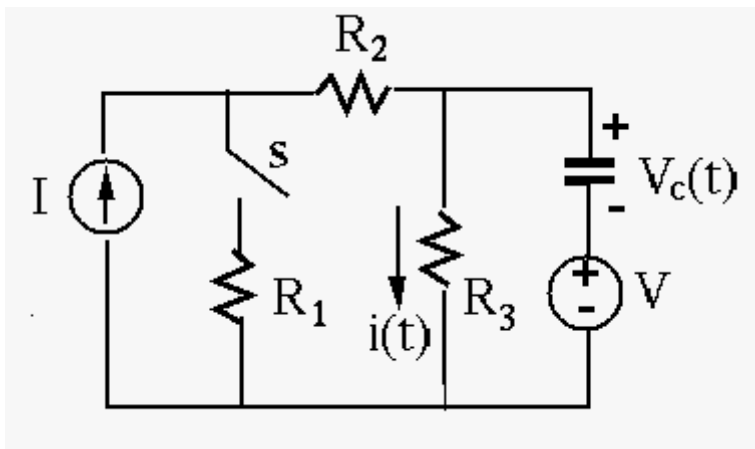3. Problem 3 (34 points)

In the circuit given below, $R_1 = R_2 = 10\text{ k}\Omega$, $R_3 = 20\text{ k}\Omega$, $C = 10\text{ }\mu\text{F}$, the current source is

$I = 1\text{ mA}$, the voltage source is $V = 10\text{ V}$. The circuit is at steady state before the switch s closes at $t = 0$. Find the current $i(t)$ through R_3 and voltage $v_c(t)$ across C for $t > 0$, and sketch them as two functions of time.



Next: [About this document ...](#) Up: [midterm2_18f](#) Previous: [Instructions](#)

Ruye Wang 2018-11-02